

## UNO

Poiché l'opamp satura a 5V e l'ampiezza di  $V_{in}$  è 1V, occorre che il modulo del guadagno sia minore di 5.

Il guadagno è del tipo  $-Z_2/Z_1$ :

$k = 1000; n = 10^{-9};$

$Z_1 = 10\text{ k}; Z_2 = 10\text{ k} + \frac{90\text{ k} \frac{1}{i 2\pi f 1\text{ n}}}{90\text{ k} + \frac{1}{i 2\pi f 1\text{ n}}}; Av = -\frac{Z_2}{Z_1}; \text{Print}["Av = ", \text{Together}[Av], " = ", \text{Apart}[Av]]$

$$Av = \frac{500000 i - 9 f \pi}{-50000 i + 9 f \pi} = -1 + \frac{450000 i}{-50000 i + 9 f \pi}$$

$\text{Simplify}[Av * \text{Conjugate}[Av], f \in \text{Reals}];$   
 $\text{Flatten}[\text{Solve}[\% = 25, f]];$   
 $\text{Last} / @ \%;$   
 $ff = \text{Select}[\%, \text{Positive}];$   
 $\text{Print}["fmin = ", \text{EngineeringForm}[ff[[1]] / 1000., 3], "kHz"]$

$$fmin = 3.13\text{kHz}$$

## DUE

$\text{dati} = \{IS \rightarrow 10^{-15}, VT \rightarrow 25 / 1000, R1 \rightarrow 20\text{ k}, R2 \rightarrow 18\text{ k}, Rc \rightarrow 1.2\text{ k}, Vcc \rightarrow 1.5\};$

$V_{eb} := \frac{Vcc - V_{in}}{R1 + R2} R2; V_{be} := \frac{V_{in} + Vcc}{R1 + R2} R2; V_{out} = Rc \left( IS e^{\frac{V_{eb}}{VT}} - IS e^{\frac{V_{be}}{VT}} \right);$

$V_{out} = Rc IS \left( e^{\frac{R2 (Vcc - V_{in})}{(R1 + R2) VT}} - e^{\frac{R2 (Vcc + V_{in})}{(R1 + R2) VT}} \right); V_{out} = Rc IS e^{\frac{R2}{(R1 + R2)} \frac{Vcc}{VT}} \left( e^{-\frac{V_{in}}{VT} \frac{R2}{(R1 + R2)}} - e^{\frac{V_{in}}{VT} \frac{R2}{(R1 + R2)}} \right);$

$V_{out} = -2 Rc IS e^{\frac{R2}{(R1 + R2)} \frac{Vcc}{VT}} \text{Sinh}\left[ \frac{R2}{(R1 + R2)} \frac{V_{in}}{VT} \right];$

$\text{Print}["Vout = ", \text{EngineeringForm}[Vout /. \text{dati}, 3]]$

$$Vout = -5.29 \text{Sinh}\left[ \frac{360 V_{in}}{19} \right]$$

$\text{Normal}[\text{Series}[Vout /. \text{dati}, \{V_{in}, 0, 1\}]];$

$\text{Print}\left["\frac{vout}{vin} = ", \text{EngineeringForm}[\% / V_{in}, 3]\right]$

$$\frac{vout}{vin} = -100.$$

$.options \text{tnom} = 16.96$

$.temp = 16.96$

$.model \text{modn} \text{npn} IS = 1\text{ fA} BF = 1000000$

$.model \text{modp} \text{pnp} IS = 1\text{ fA} BF = 1000000$

$V_{in} 10\text{ dc} 0\text{ ac} 1$

$R1p 1220\text{ k}$

$R2p 2318\text{ k}$

$R1n 1420\text{ k}$

$R2n 4518\text{ k}$

$Vcc 30 1.5$

$Vee 50 -1.5$

$Qp 623 \text{modp}$

$Qn 645 \text{modn}$

$RL 601.2\text{ k}$