

```

library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

entity controllore is
    port ( CLK      : in std_logic;
          RESET    : in std_logic;
          REQ      : in std_logic;
          CODE     : in unsigned(7 downto 0);
          DATA_IN : in unsigned(7 downto 0);
          RESULT   : out unsigned(15 downto 0);
          BUSY     : out std_logic;
          CID      : out unsigned(1 downto 0)
        );
end controllore;

architecture A of controllore is

    type stato is (idle,read_code,wait4,read_dato,wait4_bis,fine);
    signal ns,cs : stato;
    signal code_en, code_reset : std_logic;
    signal code_ck : unsigned(7 downto 0);
    signal op : std_logic;
    signal c_id : unsigned(1 downto 0);
    signal num_dati : unsigned(4 downto 0);
    signal cicli4, c4_reset, c4_en : std_logic;
    signal c4_in,c4_out : unsigned(1 downto 0);
    signal cdata_in,cdata_out : unsigned(4 downto 0);
    signal cdata_reset : std_logic;
    signal campiona, all_data, campiona_1, campiona_2: std_logic;
    signal result_en : std_logic;
    signal dato_1, dato_2 : unsigned(7 downto 0);
    signal prodotto, acc_out, acc_in, result_tmp : unsigned(15 downto 0);

begin

-----
-- 1 parte
-----

-- registro per il segnale code
process(CLK)
begin
    if CLK'event and CLK='1' then
        if (RESET='1' or code_reset = '1') then
            code_ck <= (others => '0');
        elsif code_en = '1' then
            code_ck <= code;
        end if;
    end if;
end process;

```

```
    end if;
end process;

op <= code_ck(7);
cid <= code_ck(6 downto 5);
num_dati <= code_ck(4 downto 0);

-- contatore 4 cicli
process(CLK)
begin
    if CLK'event and CLK='1' then
        if (RESET='1' or c4_reset = '1') then
            c4_out <= (others => '0');
        elsif c4_en = '1' then
            c4_out <= c4_in;
        end if;
    end if;
end process;

c4_in <= c4_out +1;
cicli4 <= '1' when c4_out = 3 else '0';

-- contatore dati letti
process(CLK)
begin
    if CLK'event and CLK='1' then
        if (RESET='1' or cdata_reset = '1') then
            cdata_out <= (others => '0');
        elsif campiona = '1' then
            cdata_out <= cdata_in;
        end if;
    end if;
end process;

cdata_in <= cdata_out +1;
all_data <= '1' when cdata_out = num_dati else '0';

-- registro di stato
process(CLK)
begin
    if CLK'event and CLK='1' then
        if RESET='1' then
            cs <= idle;
        else
            cs <= ns;
        end if;
    end if;
end process;
```

```
-- fsm combinatoria
fsm: process (cs,REQ,cicli4,all_data)
begin -- process fsm
    busy <= '1';
    code_en <= '0';
    c4_en <= '0';
    c4_reset <= '1';
    code_reset <= '0';
    campiona <= '0';
    cdata_reset <= '0';
    result_en <= '0';

    case cs is
        when idle => code_reset <= '1';
            cdata_reset <= '1';
            busy <= '0';
            if req = '1' then
                ns <= read_code;
            else
                ns <= cs;
            end if;

        when read_code => code_en <= '1';
            if req = '0' then
                ns <= wait4;
            else
                ns <= cs;
            end if;

        when wait4 => c4_en <= '1';
            c4_reset <= '0';
            if cicli4 = '1' then
                ns <= read_dato;
            else
                ns <= cs;
            end if;

        when read_dato => c4_en <= '0';
            campiona <= '1';
            ns <= wait4_bis;

        when wait4_bis => c4_en <= '1';
            c4_reset <= '0';

            if all_data = '1' then
                ns <= fine;
            else
                if cicli4 = '1' then
                    ns <= wait4; -- non ho bisogno di reesettare il
                                -- contatore perchè è a due bit
                else
                    ns <= cs;
                end if;
            end if;
    end case;
end fsm;
```

```
        end if;

        end if;

        when fine => result_en <= '1';
            ns <= idle;

        when others => null;
    end case;

end process fsm;

-----
-- 2 parte
-----

-- calcolo prodotto
process(CLK)
begin
    if CLK'event and CLK='1' then
        if (RESET='1' or op = '0') then
            dato_1 <= (others => '0');
        elsif campiona_1 = '1' then
            dato_1 <= data_in;
        end if;
    end if;
end process;

process(CLK)
begin
    if CLK'event and CLK='1' then
        if (RESET='1' or op = '0') then
            dato_2 <= (others => '0');
        elsif campiona_2 = '1' then
            dato_2 <= data_in;
        end if;
    end if;
end process;

prodotto <= dato_1 * dato_2;
campiona_1 <= '1' when (campiona = '1' and cdata_out = conv_unsigned(0,5)) else '0';
campiona_2 <= '1' when (campiona = '1' and cdata_out = conv_unsigned(1,5)) else '0';

-- calcolo media
process(CLK)
begin
    if CLK'event and CLK='1' then
        if (RESET='1' or op = '1' or result_en = '1') then
            acc_out <= (others => '0');
        elsif campiona = '1' then
            acc_out <= acc_in;
        end if;
    end if;
end process;
```

```
end process;
```

```
acc_in <= acc_out + data_in;
```

```
-- registro finale
```

```
process(CLK)
```

```
begin
```

```
  if CLK'event and CLK='1' then
```

```
    if (RESET='1') then
```

```
      result <= (others => '0');
```

```
    elsif result_en = '1' then
```

```
      result <= result_tmp;
```

```
    end if;
```

```
  end if;
```

```
end process;
```

```
result_tmp <= '0'&acc_out(15 downto 1) when (op = '0' and num_dati = 2 )
```

```
  else "00"&acc_out(15 downto 2) when (op = '0' and num_dati = 4 )
```

```
  else "000"&acc_out(15 downto 3) when (op = '0' and num_dati = 8 )
```

```
  else "0000"&acc_out(15 downto 4) when (op = '0' and num_dati = 16 )
```

```
  else "00000"&acc_out(15 downto 5) when (op = '0' and num_dati = 32 )
```

```
  else prodotto;
```

```
end A;
```