

```
library IEEE;
use IEEE.std_logic_1164.all;
use IEEE.std_logic_arith.all;
use IEEE.std_logic_unsigned.all;

entity controllore is
  port (
    CLK      : in  std_logic;
    RESET    : in  std_logic;
    PROGR    : in  std_logic;
    BUTTON   : in  std_logic;
    POS_REF  : in  unsigned(7 downto 0);
    POS_CORR : in  unsigned(7 downto 0);
    ERROR    : out unsigned(15 downto 0);
    PRENDI   : out std_logic;
    MON      : out std_logic);

end controllore;

architecture A of controllore is

  signal POS_REF_CK,error_CK, error_int : unsigned(7 downto 0);
  type stato is (idle,leggi,compara,attiva10,attiva8,attiva6,attiva4,fine);
  type stato2 is (uscita1,uscita2);
  signal cs,ns : stato;
  signal ns2,cs2 : stato2;
  signal enable_reg,reset_timer,en_timer,RESET_t, RESET_fsm : std_logic;
  signal n_count,c_count : unsigned(13 downto 0);
  signal sec10,sec8,sec6,sec4 : std_logic;
  signal n_somma,somma : unsigned(15 downto 0);

begin -- A

-- prima parte

-- registro per memorizzare posizione desiderata
process (CLK, RESET)
begin -- process
  if RESET = '1' then
    POS_REF_CK <= (others => '0');
  elsif CLK'event and CLK = '1' then -- rising clock edge
    if PROGR = '1' then
      POS_REF_CK <= POS_REF;
    end if;
  end if;
end process;

-- registro per memorizzare ERROR
process (CLK, RESET)
begin -- process
  if RESET = '1' then
    error_CK <= (others => '0');
  elsif CLK'event and CLK = '1' then -- rising clock edge
    if enable_reg = '1' then
      error_CK <= error_int;
    end if;
  end if;
end process;
```

```

-- contatore dei secondi (per semplicità 1 sec = 1 clock in simulazione)
-- 10 sec = 10000 cicli => 14 bit
process (CLK, reset_t)
begin -- process
  if RESET_t = '1' then
    c_count <= (others => '0');
  elsif CLK'event and CLK = '1' then -- rising clock edge
    if en_timer = '1' then
      c_count <= n_count;
    end if;
  end if;
end process;

n_count <= c_count + 1;
RESET_t <= RESET or reset_timer;

sec10 <= '1' when c_count = 9 else '0';
sec8 <= '1' when c_count = 7 else '0';
sec6 <= '1' when c_count = 5 else '0';
sec4 <= '1' when c_count = 3 else '0';
-- sec10 <= '1' when c_count = 9999 else '0';
-- sec8 <= '1' when c_count = 7999 else '0';
-- sec6 <= '1' when c_count = 5999 else '0';
-- sec4 <= '1' when c_count = 3999 else '0';

-- FSM
process (CLK, RESET)
begin -- process
  if RESET = '1' then
    cs <= idle;
  elsif CLK'event and CLK = '1' then -- rising clock edge
    cs <= ns;
  end if;
end process;

process (cs, PROGR, POS_REF_CK, POS_CORR, error_CK, sec10, sec8, sec6, sec4)
begin -- process

  MON <= '0';
  PRENDI <= '0';
  error_int <= conv_unsigned(0,8);
  enable_reg <= '0';
  reset_timer <= '0';
  en_timer <= '0';

  case cs is

    when idle => if PROGR = '1' then
      ns <= leggi;
    else
      ns <= cs;
    end if;

    when leggi => error_int <= POS_REF_CK - POS_CORR;
      enable_reg <= '1';
      ns <= compara;

    when compara => reset_timer <= '1';
      if error_CK = 0 then
        ns <= fine;
      end if;
  end case;
end process;

```

```
        else

            if error_CK >= 196 then
                ns <= attiva10;
            elsif error_CK >= 128 then
                ns <= attiva8;
            elsif error_CK >= 64 then
                ns <= attiva6;
            else
                ns <= attiva4;
            end if;

        end if;

    when attiva10 => en_timer <= '1';
        MON <= '1';
        if sec10 = '1' then
            ns <= leggi;
        else
            ns <= cs;
        end if;

    when attiva8 => en_timer <= '1';
        MON <= '1';
        if sec8 = '1' then
            ns <= leggi;
        else
            ns <= cs;
        end if;

    when attiva6 => en_timer <= '1';
        MON <= '1';
        if sec6 = '1' then
            ns <= leggi;
        else
            ns <= cs;
        end if;

    when attiva4 => en_timer <= '1';
        MON <= '1';
        if sec4 = '1' then
            ns <= leggi;
        else
            ns <= cs;
        end if;

    when fine => PRENDI <= '1';
        ns <= idle;

    when others => null;
end case;

end process;

-- parte seconda

-- FSM
process (CLK, RESET_fsm)
begin -- process
    if RESET_fsm = '1' then
```

```
    cs2 <= uscital;
  elsif CLK'event and CLK = '1' then -- rising clock edge
    cs2 <= ns2;
  end if;
end process;

RESET_fsm <= RESET or PROGR;

process(cs2,BUTTON,error_CK,somma)
begin -- process

  case cs2 is
    when uscital => ERROR <= conv_unsigned(error_CK,16);
      if BUTTON = '1' then
        ns2 <= uscita2;
      else
        ns2 <= cs2;
      end if;

    when uscita2 => ERROR <= somma;
      if BUTTON = '1' then
        ns2 <= uscital;
      else
        ns2 <= cs2;
      end if;

    when others => null;
  end case;

end process;

-- accumulatore della somma errori
process (CLK, RESET_fsm)
begin -- process
  if RESET_fsm = '1' then
    somma <= (others => '0');
  elsif CLK'event and CLK = '1' then -- rising clock edge
    if enable_reg = '1' then
      somma <= n_somma;
    end if;
  end if;
end process;

n_somma <= somma + conv_unsigned(error_int,16);

end A;
```