

Risoluzione 060420

$$1. V_1 = \frac{V_{CC} R_2 - V_{CC} R_1}{R_1 + R_2} = -2. V$$

$$2. I_{cn}[k+1] = \frac{V_1 + V_{CC} - V_T \log\left[\frac{I_{cn}[k]}{I_S}\right]}{R_3}$$

$$\rightarrow I_{cn} = 229 \mu A$$

$$3. I_{ep} = \frac{V_{CC}}{R_5} = 2.5 mA; I_{bp} = 100 \mu A$$

$$4. V_2 = -V_T \log\left[\frac{I_{cp}}{I_S}\right] = -770 mV$$

$$5. R_4 = \frac{V_{CC} - V_2}{I_{cn} - I_{bp}} = 44.6 k\Omega$$

$$6. g_{mn} = \frac{I_{cn}}{V_T} = 8.5 mA/V$$

$$7. g_{mp} = \frac{I_{cp}}{V_T} = 88.9 mA/V; r_{bep} = \frac{BF}{g_{mp}} = 270 \Omega$$

$$8. R_{inp} = r_{bep} + (BF+1)R_5 = 50.3 k\Omega$$

$$9. A_{vp} = \frac{(BF+1)R_5}{R_{inp}} = 0.995$$

$$10. A_{vn} = -\frac{g_{mn} \frac{R_4 R_{inp}}{R_4 + R_{inp}}}{1 + g_{mn} R_3} = -2.34$$

$$11. A_v = A_{vp} A_{vn} \frac{\frac{R_1 R_2}{R_1 + R_2} s C_a}{1 + \frac{R_1 R_2}{R_1 + R_2} s C_a} = -\frac{(2.44 \times 10^{-4}) s}{1 + (1.05 \times 10^{-4}) s}$$

$$12. R_{out} = \frac{r_{bep} + R_4}{BF + 1} = 1794.71$$

$$\text{oppure } R_{out} = \frac{r_{bep} + R_4}{BF + 1} \parallel R_5 = 945.9$$

13. Si tratta di un circuito dinamico del primo ordine e la resistenza differenziale connessa al condensatore $\left(\frac{R_1 R_2}{R_1 + R_2}\right)$ è > 0 .